





*Ответы на самостоятельную работу по физике Расчет электрических цепей*

**1 вариант**

1.

$$I_1 = 5 \text{ A}$$

$$I_2 = \text{—}$$

$$I_3 = 5 \text{ A}$$

$$I_4 = 10 \text{ A}$$

$$I_5 = 10 \text{ A}$$

$$U_1 = 100 \text{ B}$$

$$U_2 = 150 \text{ B}$$

$$U_3 = 250 \text{ B}$$

$$U_4 = 150 \text{ B}$$

$$U_5 = 100 \text{ B}$$

$$R = 50 \text{ Ом}$$

$$I = 10 \text{ A}$$

$$U = 500 \text{ B}$$

**2 вариант**

1.

$$I_1 = 10 \text{ A}$$

$$I_2 = 5 \text{ A}$$

$$I_3 = 7,5 \text{ A}$$

$$I_4 = 7,5 \text{ A}$$

$$I_5 = 7,5 \text{ A}$$

$$U_1 = 60 \text{ B}$$

$$U_2 = \text{—}$$

$$U_3 = 75 \text{ B}$$

$$U_4 = 15 \text{ B}$$

$$U_5 = 90 \text{ B}$$

$$R = 10 \text{ Ом}$$

$$I = 15 \text{ A}$$

$$U = 150 \text{ B}$$